

EEE 468 (January 2024)
VLSI Laboratory

Section: G1 Group: 02

16-bit Carry Lookahead Adder with Generate Propagate Logic

Course Instructors:

Nafis Sadik, Lecturer, BUET
Rafid Hassan Palash, Part-time Lecturer, BUET

Signature of Instructor:

Academic Honesty Statement:

IMPORTANT! Please carefully read and sign the Academic Honesty Statement, below. Type the student ID and name, and put your signature. You will not receive credit for this project experiment unless this

"In signing this statement, We hereby certify that the work on this project is our own and that we have not copied the work of any other students (past or present), and cited all relevant sources while completing this project. We understand that if we fail to honor this agreement, We will each receive a score of ZERO for this project and be subject to failure of this course."

Signature: _____

Full Name: Sheikh Abu Al Raihan

Student ID: 1906066

Signature: _____

Full Name: Kazi Abid Hasan

Student ID: 1906067

Signature: _____

Full Name: Arpa Roy Dastider

Student ID: 1906071

Signature: _____

Full Name: Ramisa Tahsin Shreya

Student ID: 1906072

Contents

1. Objectives	4
2. Design Steps	4
3. Theory	4
Theory	4
Design Cosideration	5
Circuit Diagram	6
4. Step-1 (Design Code & Directed Testbench)	6
Design Codes	6
design.sv	6
testbench.sv	8
Result	9
Waveform	9
5. Step-2 (Layered Testbench)	10
Design Codes	10
environment.sv	10
interface.sv	11
generator.sv	11
transaction.sv	12
driver.sv	12
monitor.sv	13
scoreboard.sv	13
testcases.sv	14
testbench.sv	15
Result	16
6. Step-3 (Layered Testbench with maximum coverage)	16
Design Codes	16
testbench.sv	16
testcase.sv	17
Scoreboard.sv	18
Result	21
7. Step-4 (Synthesis with Optimized Power, Performance & Area)	24

.tcl code for varying input delay	24
Data for Low Effort.....	27
Data for High & Medium Effort.....	28
Plots	29
Synthesized Design.....	31
8. Step-5 (Optimized Physical Design with respect to Die Size, Pin Planning, and Power Rails).....	32
Final design	32
Layout (After Adding Pins)	32
Layout (After Adding Power Strips)	33
Layout (Adding Rails)	33
Layout (Cell Placement)	34
Layout (After Nano Routing)	35
Layout (After Metal Fill)	36
Layout (Final).....	37
Summary Reports.....	38
Timing Report	39
DRC result	39
9. Conclusion	40
10. Links of Codes and Files	40

1. Objectives

- ❖ Design and implement a 16-bit Carry Lookahead Adder (CLA) using Generate-Propagate Logic to minimize carry propagation delay and achieve faster addition.
- ❖ Optimize critical path delay, power consumption, and area overhead for improved performance compared to traditional ripple carry adders.
- ❖ Develop a scalable and modular structure to support the design of higher-bit adders with computational efficiency.
- ❖ Conduct thorough simulation and verification using industry-standard VLSI tools to ensure accuracy, functionality, and compliance with design requirements.
- ❖ Facilitate seamless integration of the CLA design into larger arithmetic circuits, such as multipliers and ALUs, for digital system applications.

2. Design Steps

- Design Code & Directed Testbench
- Layered Testbench along with Maximum Coverage
- Synthesis
- PnR with DRC
- Optimization of PPA

3. Theory

Theory

The Carry Lookahead Adder (CLA) is a digital circuit designed to perform fast binary addition by overcoming the delay limitations of conventional adders, such as the Ripple Carry Adder. The primary challenge in binary addition is the propagation of carry bits, which increases the computational delay as the number of bits increases. The CLA addresses this challenge by using Generate and Propagate logic to predict the carry at each bit position independently, significantly reducing the delay.

In the CLA, the Generate (G) and Propagate (P) signals are calculated for each bit based on the input bits:

- **Generate (G):** Indicates if a carry is generated at a specific bit position. It is calculated as $G_i = A_i \cdot B_i$, where A and B are the input bits.
- **Propagate (P):** Indicates if a carry from a previous bit will propagate through the current bit position. It is calculated as $P_i = A_i + B_i$

Using these signals, the carry for each bit position can be computed directly as: $C_{i+1} = G_i + (P_i \cdot C_i)$. This eliminates the need for the carry to sequentially propagate through all bit positions, as seen in the Ripple Carry Adder. The addition operation is completed by combining the carry signals with the sum logic: $S_i = P_i \oplus C_i$

Design Cosideration

The conventional 16-bit CLA designed with 4 blocks of 4-bit CLAs (chain CLA) introduce a delay of 13 gate level where a block cannot calculate the sum bits before untill the carry out of previous block is calculated. Hence, the circuit is designed in a hierarchical manner to ensure scalability and timing. Groups of bits are processed simultaneously, further reducing the overall delay.


The hierarchical structure of carry lookahead generators is designed to optimize the computation of carries in binary addition. In a 16-bit adder, there are three "floors" of generators:

1. **First Floor (16 Sum Components):**
 - Each component adds two bits and computes the propagated and generated carry indicators.
 - The result bit is computed once the carry from the previous component is available.
2. **Second Floor (Four 4-bit Carry Lookahead Generators):**
 - These generators calculate the carries quickly based on the inputs from the previous floor's components.
 - The carries are computed using a two-level logic structure, where the carry propagation and generation indicators from the previous floor determine the carries.
3. **Third Floor (One Carry Lookahead Generator):**
 - This generator computes the input carries for the second-floor generators and the propagated and generated carry indicators for the entire 16-bit adder.
 - These outputs are used to compute the overall carry of the adder or passed as inputs to higher floors, such as for a 64-bit adder.

The delay of this structure is significantly reduced compared to ripple carry adders and chains of CLA adders. The total delay is 8 gate level (1+2+2+2+1), with each floor contributing a delay of up to 4 gate levels. The delay is proportional to the number of floors, approximately $\log_4 n$ for an n-bit adder, making it much faster.

Design Logic	Gate level Delay
Chain CLA	13
Hierarchical CLA	8

Circuit Diagram

 

4. Step-1 (Design Code & Directed Testbench)

Design Codes

design.sv

```

module cla16 (
    input clk,
    input [15:0] A,
    input [15:0] B,
    input Cin,
    output reg [15:0] Sum,
    output reg Cout
);

    reg [3:0] P_block, G_block; // 4-bit Block propagate and generate
    reg [3:0] C_block; // 4-bit Block carry
    reg [15:0] P, G; // Bit propagate and generate

    always@(posedge clk) begin
        // Bit Propagate (P) and Generate (G) (1st floor)
        P = A ^ B;
        G = A & B;

        // 4-bit CLA Generators for each block (2nd Floor)
        cla_4bit_generator(P[3:0], G[3:0], P_block[0], G_block[0]);
        cla_4bit_generator(P[7:4], G[7:4], P_block[1], G_block[1]);
    end

```

```

        cla_4bit_generator(P[11:8],G[11:8],P_block[2],G_block[2]);
        cla_4bit_generator(P[15:12],G[15:12],P_block[3],G_block[3]);

// Block and final Carry Logic (3rd floor)
        carry_block_generator(P_block,G_block,Cin,C_block,Cout);

// Compute carry signals (2nd floor) and sum (1st floor)
        bit_sum(P[3:0],G[3:0],C_block[0],Sum[3:0]);
        bit_sum(P[7:4],G[7:4],C_block[1],Sum[7:4]);
        bit_sum(P[11:8],G[11:8],C_block[2],Sum[11:8]);
        bit_sum(P[15:12],G[15:12],C_block[3],Sum[15:12]);
end

task cla_4bit_generator (
    input [3:0] P,
    input [3:0] G,
    output reg P_block,
    output reg G_block
);
begin
    P_block = (P[3] & P[2] & P[1] & P[0]);
    G_block = (G[3] | (P[3] & G[2]) | (P[3] & P[2] & G[1]) | (P[3] & P[2] & P[1] & G[0]));
end
endtask

task carry_block_generator (
    input [3:0] P,
    input [3:0] G,
    input Cin,
    output reg [3:0] C,
    output reg Cout
);
begin
    // Compute block carries
    C[0] = Cin;
    C[1] = (G[0] | (P[0] & C[0]));
    C[2] = (G[1] | (P[1] & C[1]));
    C[3] = (G[2] | (P[2] & C[2]));

    // Compute final carry-out
    Cout = (G[3] | (P[3] & C[3]));
end
endtask

task bit_sum (
    input [3:0] P,G,
    input Cin,
    output reg [3:0] Sum
);

```

```

begin
    Sum[0]=(P[0]^Cin);
    Sum[1]=(P[1]^(G[0]|(P[0]&Cin)));
    Sum[2]=(P[2]^(G[1]|(G[0]&P[1])|(P[0]&P[1]&Cin)));
    Sum[3]=(P[3]^(G[2]|(G[1]&P[2])|(G[0]&P[2]&P[1])|(P[0]&P[1]&P[2]&Cin)));
end
endtask
endmodule

```

testbench.sv

```

module cla16_tb;
    reg clk;
    reg [15:0] A, B;
    reg Cin;
    wire [15:0] Sum;
    wire Cout;

    reg [16:0] reference_sum;

    initial begin
        clk=0;
        forever #5 clk=~clk;
    end

    cla16 dut (
        .A(A),
        .B(B),
        .Cin(Cin),
        .clk(clk),
        .Sum(Sum),
        .Cout(Cout)
    );

    initial begin
        test(16'h0000, 16'h0000, 1'b0);
        test(16'h0001, 16'h0001, 1'b0);
        test(16'hFFFF, 16'h0001, 1'b0);
        test(16'hAAAA, 16'h5555, 1'b1);
        test(16'h1234, 16'h5678, 1'b1);
        test(16'hFFFF, 16'hFFFF, 1'b1);
        $display("Simulation complete.");
        $finish;
    end

    initial begin

```



```

$dumpfile("cla16.vcd");
$dumpvars;
end
task test(input [15:0] A_in, B_in, input Cin_in);
begin
    A = A_in;
    B = B_in;
    Cin = Cin_in;
    #10;
    reference_sum = A + B + Cin;
    if ((Sum!=reference_sum[15:0])||(Cout != reference_sum[16]))
        $display("Test Failed: A=%h, B=%h, Cin=%b | Expected Sum=%h, Cout=%b | Resulted
Sum=%h, Cout=%b",
            A, B, Cin, reference_sum[15:0], reference_sum[16], Sum, Cout);
    else
        $display("Test Passed: A=%h, B=%h, Cin=%b | Expected Sum=%h, Cout=%b | Resulted
Sum=%h, Cout=%b",
            A, B, Cin, reference_sum[15:0], reference_sum[16], Sum, Cout);
    end
endtask
endmodule

```

Result

```

xcelium> run
Test Passed: A=0000, B=0000, Cin=0 | Expected Sum=0000, Cout=0 | Resulted Sum=0000, Cout=0
Test Passed: A=0001, B=0001, Cin=0 | Expected Sum=0002, Cout=0 | Resulted Sum=0002, Cout=0
Test Passed: A=ffff, B=0001, Cin=0 | Expected Sum=0000, Cout=1 | Resulted Sum=0000, Cout=1
Test Passed: A=aaaa, B=5555, Cin=1 | Expected Sum=0000, Cout=1 | Resulted Sum=0000, Cout=1
Test Passed: A=1234, B=5678, Cin=1 | Expected Sum=68ad, Cout=0 | Resulted Sum=68ad, Cout=0
Test Passed: A=ffff, B=ffff, Cin=1 | Expected Sum=ffff, Cout=1 | Resulted Sum=ffff, Cout=1
Simulation complete.
Simulation complete via $finish(1) at time 60 NS + 0

```

All test cases passed successfully.

Waveform



5. Step-2 (Layered Testbench)

Design Codes

environment.sv

```
`include "generator.sv"
`include "driver.sv"
`include "monitor.sv"
`include "scoreboard.sv"
class environment;

    mailbox gen2drv;
    mailbox drv2sb;
    mailbox mon2sb;

    generator gen;
    driver drv;
    monitor mon;
    scoreboard scb;

    event driven;
    virtual cla_if claif;
    function new (virtual cla_if claif);
        this.claif=claif;
        gen2drv=new();
        drv2sb=new();
        mon2sb=new();
        gen=new(generator(gen2drv));
        drv=new(driver(gen2drv, drv2sb, claif.DRIVER, driven));
        mon=new (monitor(mon2sb, claif.MONITOR, driven));
        scb=new(scoreboard(drv2sb,mon2sb));
    endfunction

    task main(input int count);
        fork gen.main(count);
            drv.main(count);
            mon.main(count);
            scb.main(count);
        join
        $finish;
    endtask:main

endclass: environment
```

interface.sv

```
interface cla_if (input clk);
    logic [15:0] a,b;
    logic cin;
    logic [15:0] sum;
    logic cout;

    clocking driver_cb @(negedge clk); default input #1 output #1;
        output a, b,cin;
    endclocking

    clocking mon_cb @(negedge clk); default input #1 output #1;
        input a,b,cin;
        input sum,cout;
    endclocking

    modport DRIVER (clocking driver_cb, input clk);
    modport MONITOR (clocking mon_cb, input clk);
endinterface
```

generator.sv

```
`include "transaction.sv"
class generator;
mailbox gen2driv;
transaction g_trans, custom_trans;
function new (mailbox gen2driv);
this.gen2driv=gen2driv;
endfunction
task main(input int count);
repeat(count) begin
    g_trans=new();
    g_trans=new custom_trans;
    assert(g_trans.randomize());
    gen2driv.put(g_trans);
end
endtask: main
endclass:generator
```

transaction.sv

```
class transaction;
  rand bit [15:0] a;
  rand bit [15:0] b;
  rand bit cin;
  bit [15:0] sum;
  bit cout;
endclass:transaction
```

driver.sv

```
class driver;
  mailbox gen2driv, driv2sb;
  virtual cla_if.DRIVER claif;
  transaction d_trans;
  event driven;

  function new (mailbox gen2driv, driv2sb, virtual cla_if.DRIVER claif, event driven);
    this.gen2driv=gen2driv;
    this.claif=claif;
    this.driven=driven;
    this.driv2sb=driv2sb;
  endfunction

  task main(input int count);
  repeat(count) begin
    d_trans=new();
    gen2driv.get(d_trans);
    @(claif.driver_cb);
    claif.driver_cb.a <= d_trans.a;
    claif.driver_cb.b <= d_trans.b;
    claif.driver_cb.cin <= d_trans.cin;
    driv2sb.put(d_trans);
    -> driven;
  end
  endtask:main
endclass:driver
```

monitor.sv

```
class monitor;

    mailbox mon2sb;
    virtual cla_if.MONITOR claif;
    transaction m_trans;
    event driven;
    function new(mailbox mon2sb, virtual cla_if.MONITOR claif, event driven);
        this.mon2sb=mon2sb;
        this.claif=claif;
        this.driven=driven;
    endfunction

    task main(input int count);
        @(driven);
        @(claif.mon_cb); repeat(count) begin
            m_trans=new();
            @(posedge claif.clk);
            m_trans.cout=claif.mon_cb.cout;
            m_trans.sum=claif.mon_cb.sum;
            mon2sb.put(m_trans);
        end
    endtask:main
endclass: monitor
```

scoreboard.sv

```
class scoreboard;

    mailbox driv2sb;
    mailbox mon2sb;

    transaction d_trans;
    transaction m_trans;
    event driven;

    function new(mailbox driv2sb, mon2sb);
        this.driv2sb=driv2sb;
        this.mon2sb=mon2sb;
    endfunction

    task main(input int count);
        $display("--Scoreboard Test Starts- -");
        repeat(count) begin
```

```

    m_trans=new();
    mon2sb.get(m_trans);
    report();
    if((m_trans.sum != d_trans.sum)|| (m_trans.cout != d_trans.cout))
        $display("Failed : a=%d b=%d cin=%d Expected sum=%d Resulted sum=%d Expected
cout=%d Resulted cout=%d",d_trans.a,d_trans.b, d_trans.cin,d_trans.sum, m_trans.sum,d_trans.cout,
m_trans.cout);
    else
        $display("Passed : a=%d b=%d cin=%d Expected sum=%d Resulted sum=%d Expected
cout=%d Resulted cout=%d",d_trans.a,d_trans.b, d_trans.cin,d_trans.sum, m_trans.sum,d_trans.cout,
m_trans.cout);
    end
    $display("--Scoreboard Test Ends---");
endtask:main

task report();
    d_trans=new();
    driv2sb.get(d_trans);
    {d_trans.cout,d_trans.sum}=d_trans.a+d_trans.b+d_trans.cin;
endtask: report

endclass:scoreboard

```

testcases.sv

```

`include "environment.sv"

program test(input int count, cla_if claif);
    environment env;

    class testcase01 extends transaction;
        //constraint c_s {
            //s inside {[0:1], [14:15]};
            //s inside {[0:15]};
        //}
    endclass:testcase01

    initial begin
        testcase01 testcase01handle;
        testcase01handle=new();

        env=new(claif);
        env.gen.custom_trans=testcase01handle;
        env.main(count);
    end

endprogram:test

```

testbench.sv

```
`include "testcase01.sv"
`include "test.sv"
`include "interface.sv"

module testbench;
    bit clk;

    initial begin
        forever #5 clk =~clk;
    end

    int count=15;
    cla_if claif(clk);

    test test01(count,claif);

    initial begin
        $dumpfile("dump.vcd");
        $dumpvars;
    end

    cla16 DUT (
        .A(claif.a),
        .B(claif.b),
        .Cin(claif.cin),
        .Sum(claif.sum),
        .Cout(claif.cout),
        .clk(clk)
    );

Endmodule
```

Result

```
xcelium> run
--Scoreboard Test Starts- -
Passed : a=44355 b=43013 cin=1 Expected sum=21833 Resulted sum=21833 Expected cout=1 Resulted cout=1
Passed : a=41469 b=52620 cin=0 Expected sum=28553 Resulted sum=28553 Expected cout=1 Resulted cout=1
Passed : a=12353 b=56112 cin=0 Expected sum= 2929 Resulted sum= 2929 Expected cout=1 Resulted cout=1
Passed : a=58832 b=24293 cin=0 Expected sum=17589 Resulted sum=17589 Expected cout=1 Resulted cout=1
Passed : a= 3543 b=47486 cin=0 Expected sum=51029 Resulted sum=51029 Expected cout=0 Resulted cout=0
Passed : a= 2514 b=55943 cin=0 Expected sum=58457 Resulted sum=58457 Expected cout=0 Resulted cout=0
Passed : a=60864 b=10667 cin=0 Expected sum= 5995 Resulted sum= 5995 Expected cout=1 Resulted cout=1
Passed : a= 3789 b=20499 cin=0 Expected sum=24288 Resulted sum=24288 Expected cout=0 Resulted cout=0
Passed : a=43633 b=29258 cin=0 Expected sum= 7355 Resulted sum= 7355 Expected cout=1 Resulted cout=1
Passed : a=49535 b= 3810 cin=1 Expected sum=53346 Resulted sum=53346 Expected cout=0 Resulted cout=0
Passed : a= 9418 b=39227 cin=1 Expected sum=48646 Resulted sum=48646 Expected cout=0 Resulted cout=0
Passed : a=14360 b= 6313 cin=0 Expected sum=20673 Resulted sum=20673 Expected cout=0 Resulted cout=0
Passed : a=26358 b=17563 cin=1 Expected sum=43922 Resulted sum=43922 Expected cout=0 Resulted cout=0
Passed : a=14075 b=57862 cin=1 Expected sum= 6402 Resulted sum= 6402 Expected cout=1 Resulted cout=1
Passed : a=27634 b=49218 cin=0 Expected sum=11316 Resulted sum=11316 Expected cout=1 Resulted cout=1
--Scoreboard Test Ends---
Simulation complete via $finish(1) at time 165 NS + 2
./environment.sv:35      $finish;
xcelium> exit
```

All random test cases passed successfully.

6. Step-3 (Layered Testbench with maximum coverage)

Design Codes

testbench.sv

```
`include "testcase01.sv"
//`include "test.sv"
`include "interface.sv"

module testbench;
    bit clk;

    initial begin
        forever #5 clk =~clk;
    end

    int count=500;
    cla_if claif(clk);

    test test01(count,claif);
```



```

initial begin
    $dumpfile("dump.vcd");
    $dumpvars;
    #10000;
    $finish;
end

```

```

cla16 DUT (
    .A(claif.a),
    .B(claif.b),
    .Cin(claif.cin),
    .Sum(claif.sum),
    .Cout(claif.cout),
    .clk(clk)
);

```

```

Endmodule

```

testcase.sv

```

`include "environment.sv"

```

```

program test(input int count, cla_if claif);
    environment env;

```

```

class testcase01 extends transaction;
    constraint c_s {
        a inside {[0:65535]};
        b inside {[0:65535]};
        cin inside {[0:1]};
    }

```

```

endclass:testcase01

```

```

initial begin
    testcase01 testcase01handle;
    testcase01handle=new();

    env=new(claif);
    env.gen.custom_trans=testcase01handle;
    env.main(count);
end

```

```

endprogram:test

```

Scoreboard.sv

```
class scoreboard;

    mailbox driv2sb;
    mailbox mon2sb;

    transaction d_trans;
    transaction m_trans;

    logic V;

    real Flags [4] = '{default:64'b0};
    real Pass [4] = '{default:64'b0};
    real Total_Pass;
    real Fail [4] = '{default:64'b0};
    real pc [4], f_pc [4], p_pc [4];
    logic [1:0] X,Y;

    event driven;

    function new(mailbox driv2sb, mon2sb);
        this.driv2sb=driv2sb;
        this.mon2sb=mon2sb;
    endfunction

    task main(input int count);
        $display("--Scoreboard Test Starts- -");
        repeat(count) begin
            m_trans=new();
            mon2sb.get(m_trans);
            report();

            Y = {d_trans.cout, V};
            if((m_trans.sum != d_trans.sum)|| (m_trans.cout != d_trans.cout))
                begin
                    $display("Failed : a=%d b=%d cin=%d Expected sum=%d Resulted sum=%d Expected
cout=%d Resulted cout=%d",d_trans.a,d_trans.b, d_trans.cin,d_trans.sum, m_trans.sum,d_trans.cout,
m_trans.cout);
                    if(Y==2'b00)
                        Fail[0] = Fail[0]+1;
                    else if(Y==2'b01)
                        Fail[1] = Fail[1]+1;
                    else if(Y==2'b10)
                        Fail[2] = Fail[2]+1;
                    else if(Y==2'b11)
                        Fail[3] = Fail[3]+1;
                end
        end
    endtask
endclass
```

```

else
begin
    $display("Passed : a=%d b=%d cin=%d Expected sum=%d Resulted sum=%d Expected
cout=%d Resulted cout=%d",d_trans.a,d_trans.b, d_trans.cin,d_trans.sum, m_trans.sum,d_trans.cout,
m_trans.cout);
    if(Y==2'b00)
        Pass[0] = Pass[0]+1;
    else if(Y==2'b01)
        Pass[1] = Pass[1]+1;
    else if(Y==2'b10)
        Pass[2] = Pass[2]+1;
    else if(Y==2'b11)
        Pass[3] = Pass[3]+1;
    end
end

pc[0]=(Flags[0]*100)/count;
pc[1]=(Flags[1]*100)/count;
pc[2]=(Flags[2]*100)/count;
pc[3]=(Flags[3]*100)/count;

p_pc[0]=(Pass[0]*100)/Flags[0];
p_pc[1]=(Pass[1]*100)/Flags[1];
p_pc[2]=(Pass[2]*100)/Flags[2];
p_pc[3]=(Pass[3]*100)/Flags[3];

f_pc[0]=(Fail[0]*100)/Flags[0];
f_pc[1]=(Fail[1]*100)/Flags[1];
f_pc[2]=(Fail[2]*100)/Flags[2];
f_pc[3]=(Fail[3]*100)/Flags[3];

Total_Pass=((Pass[0]+Pass[1]+Pass[2]+Pass[3])*100)/count;

//$display("--Scoreboard Test Ends---");

$display("\n\n-----Coverage Results-----\n\n");

$display("# of Case Tested for Type 1: {CV}='00'=%0.0f cases with percentage=%f, Pass rate=%f,
Fail rate=%f",Flags[0],pc[0],p_pc[0],f_pc[0]);
$display("# of Case Tested for Type 2: {CV}='01'=%0.0f cases with percentage=%f, Pass rate=%f,
Fail rate=%f",Flags[1],pc[1],p_pc[1],f_pc[1]);
$display("# of Case Tested for Type 3: {CV}='10'=%0.0f cases with percentage=%f, Pass rate=%f,
Fail rate=%f",Flags[2],pc[2],p_pc[2],f_pc[2]);
$display("# of Case Tested for Type 4: {CV}='11'=%0.0f cases with percentage=%f, Pass rate=%f,

```

```

Fail rate=%f",Flags[3],pc[3],p_pc[3],f_pc[3]);
    $display("Total Coverage pass rate = %0.2f %%\n",Total_Pass);

    $display("\n\n-----Coverage Results End-----\n\n");

endtask:main

task report();
    d_trans=new();
    driv2sb.get(d_trans);
    {d_trans.cout,d_trans.sum}=d_trans.a+d_trans.b+d_trans.cin;

    if(d_trans.cout == 1)
        V = 1'b1;
    else
        V = 1'b0;

    X = {d_trans.cout, V};

    if(X==2'b00)
        Flags[0] = Flags[0]+1;
    else if(X==2'b01)
        Flags[1] = Flags[1]+1;
    else if(X==2'b10)
        Flags[2] = Flags[2]+1;
    else if(X==2'b11)
        Flags[3] = Flags[3]+1;

endtask: report

endclass:scoreboard

```

Result

```
Loading snapshot worklib.testbench:sv ..... Done
SVSEED set randomly from command line: 1108104969
ncsim> source /home/eda/cadence/lux/INCISIV/icd/icdcm_tib_016/flow/INCISIV/INCISIV151/15.10.015/lux86/tools/inca/files/ncsimrc
ncsim> run
--Scoreboard Test Starts--
Passed : a=12448 b=34045 cin=0 Expected sum=46493 Resulted sum=46493 Expected cout=0 Resulted cout=0
Passed : a=29794 b=13468 cin=0 Expected sum=43262 Resulted sum=43262 Expected cout=0 Resulted cout=0
Passed : a= 7873 b= 7039 cin=0 Expected sum=14912 Resulted sum=14912 Expected cout=0 Resulted cout=0
Passed : a= 4151 b=36008 cin=1 Expected sum=40160 Resulted sum=40160 Expected cout=0 Resulted cout=0
Passed : a=54132 b= 8293 cin=1 Expected sum=62426 Resulted sum=62426 Expected cout=0 Resulted cout=0
Passed : a= 8957 b=44858 cin=0 Expected sum=53815 Resulted sum=53815 Expected cout=0 Resulted cout=0
Passed : a=52346 b=29001 cin=1 Expected sum=15812 Resulted sum=15812 Expected cout=1 Resulted cout=1
Passed : a=15594 b=31701 cin=0 Expected sum=47295 Resulted sum=47295 Expected cout=0 Resulted cout=0
Passed : a=16379 b=38650 cin=1 Expected sum=55030 Resulted sum=55030 Expected cout=0 Resulted cout=0
Passed : a=29658 b=15326 cin=0 Expected sum=44984 Resulted sum=44984 Expected cout=0 Resulted cout=0
Passed : a=64097 b=16467 cin=1 Expected sum=15029 Resulted sum=15029 Expected cout=1 Resulted cout=1
Passed : a=13934 b=54287 cin=0 Expected sum= 2685 Resulted sum= 2685 Expected cout=1 Resulted cout=1
Passed : a=65329 b=20638 cin=0 Expected sum=20431 Resulted sum=20431 Expected cout=1 Resulted cout=1
Passed : a=16965 b= 5152 cin=1 Expected sum=22118 Resulted sum=22118 Expected cout=0 Resulted cout=0
Passed : a=13693 b=64996 cin=1 Expected sum=13154 Resulted sum=13154 Expected cout=1 Resulted cout=1
Passed : a=53734 b=49438 cin=1 Expected sum=37637 Resulted sum=37637 Expected cout=1 Resulted cout=1
Passed : a=23435 b= 5887 cin=1 Expected sum=29323 Resulted sum=29323 Expected cout=0 Resulted cout=0
Passed : a= 7829 b=53111 cin=1 Expected sum=60941 Resulted sum=60941 Expected cout=0 Resulted cout=0
Passed : a= 9883 b=18810 cin=0 Expected sum=28693 Resulted sum=28693 Expected cout=0 Resulted cout=0
Passed : a=46623 b=13114 cin=1 Expected sum=59738 Resulted sum=59738 Expected cout=0 Resulted cout=0
Passed : a=47358 b=19655 cin=0 Expected sum= 1477 Resulted sum= 1477 Expected cout=1 Resulted cout=1
Passed : a=49141 b=16263 cin=0 Expected sum=65404 Resulted sum=65404 Expected cout=0 Resulted cout=0
Passed : a=32043 b=62585 cin=0 Expected sum=29092 Resulted sum=29092 Expected cout=1 Resulted cout=1
Passed : a=37667 b= 3761 cin=1 Expected sum=41429 Resulted sum=41429 Expected cout=0 Resulted cout=0
Passed : a=47939 b= 6211 cin=0 Expected sum=54150 Resulted sum=54150 Expected cout=0 Resulted cout=0
Passed : a=55654 b=28584 cin=1 Expected sum=18703 Resulted sum=18703 Expected cout=1 Resulted cout=1
Passed : a=46779 b=58943 cin=1 Expected sum=40187 Resulted sum=40187 Expected cout=1 Resulted cout=1
Passed : a=62089 b=53181 cin=0 Expected sum=49734 Resulted sum=49734 Expected cout=1 Resulted cout=1
Passed : a=37007 b=59636 cin=0 Expected sum=31107 Resulted sum=31107 Expected cout=1 Resulted cout=1
Passed : a=18132 b=23311 cin=0 Expected sum=41443 Resulted sum=41443 Expected cout=0 Resulted cout=0
Passed : a=65214 b= 3428 cin=1 Expected sum= 3107 Resulted sum= 3107 Expected cout=1 Resulted cout=1
Passed : a=39471 b=27649 cin=0 Expected sum= 1584 Resulted sum= 1584 Expected cout=1 Resulted cout=1
Passed : a=36968 b=63811 cin=0 Expected sum=35243 Resulted sum=35243 Expected cout=1 Resulted cout=1
Passed : a=17079 b= 8320 cin=1 Expected sum=25400 Resulted sum=25400 Expected cout=0 Resulted cout=0
Passed : a=36198 b=49831 cin=1 Expected sum=20494 Resulted sum=20494 Expected cout=1 Resulted cout=1
Passed : a=18116 b= 842 cin=0 Expected sum=18958 Resulted sum=18958 Expected cout=0 Resulted cout=0
Passed : a= 8230 b=52997 cin=1 Expected sum=61228 Resulted sum=61228 Expected cout=0 Resulted cout=0
Passed : a=50483 b=49896 cin=1 Expected sum=34844 Resulted sum=34844 Expected cout=1 Resulted cout=1
Passed : a=57743 b=53002 cin=0 Expected sum=45209 Resulted sum=45209 Expected cout=1 Resulted cout=1
Passed : a=38875 b=25768 cin=0 Expected sum=64643 Resulted sum=64643 Expected cout=0 Resulted cout=0
Passed : a= 8258 b=34441 cin=1 Expected sum=42700 Resulted sum=42700 Expected cout=0 Resulted cout=0
Passed : a=23588 b=40481 cin=1 Expected sum=64070 Resulted sum=64070 Expected cout=0 Resulted cout=0
Passed : a=64859 b=56153 cin=1 Expected sum=55477 Resulted sum=55477 Expected cout=1 Resulted cout=1
Passed : a=16488 b=19545 cin=0 Expected sum=36033 Resulted sum=36033 Expected cout=0 Resulted cout=0
Passed : a=33474 b=12236 cin=1 Expected sum=45711 Resulted sum=45711 Expected cout=0 Resulted cout=0
```

Passed : a=64875 b=19262 cin=0	Expected sum=18601	Resulted sum=18601	Expected cout=1	Resulted cout=1
Passed : a=42263 b=20732 cin=0	Expected sum=62995	Resulted sum=62995	Expected cout=0	Resulted cout=0
Passed : a=15315 b= 3606 cin=1	Expected sum=18922	Resulted sum=18922	Expected cout=0	Resulted cout=0
Passed : a=26534 b=32419 cin=0	Expected sum=58953	Resulted sum=58953	Expected cout=0	Resulted cout=0
Passed : a=37690 b= 6826 cin=0	Expected sum=44516	Resulted sum=44516	Expected cout=0	Resulted cout=0
Passed : a=52987 b=44479 cin=1	Expected sum=31931	Resulted sum=31931	Expected cout=1	Resulted cout=1
Passed : a=65108 b=19808 cin=1	Expected sum=19381	Resulted sum=19381	Expected cout=1	Resulted cout=1
Passed : a=38950 b= 2714 cin=1	Expected sum=39665	Resulted sum=39665	Expected cout=0	Resulted cout=0
Passed : a=47376 b= 9620 cin=0	Expected sum=56996	Resulted sum=56996	Expected cout=0	Resulted cout=0
Passed : a=36139 b=26581 cin=0	Expected sum=62720	Resulted sum=62720	Expected cout=0	Resulted cout=0
Passed : a=44012 b=36271 cin=0	Expected sum=14747	Resulted sum=14747	Expected cout=1	Resulted cout=1
Passed : a=44727 b=15260 cin=1	Expected sum=59988	Resulted sum=59988	Expected cout=0	Resulted cout=0
Passed : a=38090 b=63878 cin=0	Expected sum=36432	Resulted sum=36432	Expected cout=1	Resulted cout=1
Passed : a=18906 b= 5274 cin=0	Expected sum=24180	Resulted sum=24180	Expected cout=0	Resulted cout=0
Passed : a=40168 b=51621 cin=0	Expected sum=26253	Resulted sum=26253	Expected cout=1	Resulted cout=1
Passed : a=61088 b=41463 cin=1	Expected sum=37016	Resulted sum=37016	Expected cout=1	Resulted cout=1
Passed : a=18262 b=34577 cin=1	Expected sum=52840	Resulted sum=52840	Expected cout=0	Resulted cout=0
Passed : a=39491 b=20554 cin=1	Expected sum=60046	Resulted sum=60046	Expected cout=0	Resulted cout=0
Passed : a=16251 b=44719 cin=1	Expected sum=60971	Resulted sum=60971	Expected cout=0	Resulted cout=0
Passed : a=57900 b=16472 cin=1	Expected sum= 8837	Resulted sum= 8837	Expected cout=1	Resulted cout=1
Passed : a=60332 b=58771 cin=0	Expected sum=53567	Resulted sum=53567	Expected cout=1	Resulted cout=1
Passed : a=19764 b=59687 cin=0	Expected sum=13915	Resulted sum=13915	Expected cout=1	Resulted cout=1
Passed : a=38011 b=26302 cin=1	Expected sum=64314	Resulted sum=64314	Expected cout=0	Resulted cout=0
Passed : a=64931 b=57199 cin=0	Expected sum=56594	Resulted sum=56594	Expected cout=1	Resulted cout=1
Passed : a=50362 b=41140 cin=0	Expected sum=25966	Resulted sum=25966	Expected cout=1	Resulted cout=1
Passed : a=43121 b=53870 cin=0	Expected sum=31455	Resulted sum=31455	Expected cout=1	Resulted cout=1
Passed : a=19901 b=55318 cin=1	Expected sum= 9684	Resulted sum= 9684	Expected cout=1	Resulted cout=1
Passed : a=23683 b=45743 cin=0	Expected sum= 3890	Resulted sum= 3890	Expected cout=1	Resulted cout=1
Passed : a= 5915 b=25037 cin=1	Expected sum=30953	Resulted sum=30953	Expected cout=0	Resulted cout=0
Passed : a=16419 b=63911 cin=0	Expected sum=14794	Resulted sum=14794	Expected cout=1	Resulted cout=1
Passed : a=50755 b=11811 cin=0	Expected sum=62566	Resulted sum=62566	Expected cout=0	Resulted cout=0
Passed : a=50662 b=29480 cin=0	Expected sum=14606	Resulted sum=14606	Expected cout=1	Resulted cout=1
Passed : a=62009 b=43050 cin=0	Expected sum=39523	Resulted sum=39523	Expected cout=1	Resulted cout=1
Passed : a=58972 b=10471 cin=0	Expected sum= 3907	Resulted sum= 3907	Expected cout=1	Resulted cout=1
Passed : a=58154 b= 7475 cin=1	Expected sum= 94	Resulted sum= 94	Expected cout=1	Resulted cout=1
Passed : a=29359 b=56208 cin=1	Expected sum=20032	Resulted sum=20032	Expected cout=1	Resulted cout=1
Passed : a=22538 b=36940 cin=0	Expected sum=59478	Resulted sum=59478	Expected cout=0	Resulted cout=0
Passed : a=14249 b=32239 cin=1	Expected sum=46489	Resulted sum=46489	Expected cout=0	Resulted cout=0
Passed : a= 643 b= 4273 cin=0	Expected sum= 4916	Resulted sum= 4916	Expected cout=0	Resulted cout=0
Passed : a=61186 b=36470 cin=1	Expected sum=32121	Resulted sum=32121	Expected cout=1	Resulted cout=1
Passed : a=30653 b= 4487 cin=0	Expected sum=35140	Resulted sum=35140	Expected cout=0	Resulted cout=0
Passed : a= 2118 b=60559 cin=0	Expected sum=62677	Resulted sum=62677	Expected cout=0	Resulted cout=0
Passed : a=59506 b=32725 cin=0	Expected sum=26695	Resulted sum=26695	Expected cout=1	Resulted cout=1
Passed : a=37843 b=57030 cin=1	Expected sum=29338	Resulted sum=29338	Expected cout=1	Resulted cout=1
Passed : a=26760 b=27730 cin=0	Expected sum=54490	Resulted sum=54490	Expected cout=0	Resulted cout=0
Passed : a= 719 b=60468 cin=0	Expected sum=61187	Resulted sum=61187	Expected cout=0	Resulted cout=0
Passed : a= 3312 b=61811 cin=1	Expected sum=65124	Resulted sum=65124	Expected cout=0	Resulted cout=0
Passed : a= 9191 b=59445 cin=0	Expected sum= 3100	Resulted sum= 3100	Expected cout=1	Resulted cout=1
Passed : a=21646 b=25963 cin=0	Expected sum=47609	Resulted sum=47609	Expected cout=0	Resulted cout=0
Passed : a=13903 b=41195 cin=1	Expected sum=55099	Resulted sum=55099	Expected cout=0	Resulted cout=0

16-bit Carry Lookahead Adder with Generate Propagate Logic

Passed : a=63945 b=56721 cin=0	Expected sum=55130	Resulted sum=55130	Expected cout=1	Resulted cout=1
Passed : a=40767 b=29003 cin=1	Expected sum= 4235	Resulted sum= 4235	Expected cout=1	Resulted cout=1
Passed : a=58313 b=54891 cin=0	Expected sum=47668	Resulted sum=47668	Expected cout=1	Resulted cout=1
Passed : a=40627 b= 6939 cin=1	Expected sum=47567	Resulted sum=47567	Expected cout=0	Resulted cout=0
Passed : a=37317 b= 2905 cin=0	Expected sum=40222	Resulted sum=40222	Expected cout=0	Resulted cout=0
Passed : a=60786 b=25912 cin=1	Expected sum=21163	Resulted sum=21163	Expected cout=1	Resulted cout=1
Passed : a=17992 b=45078 cin=0	Expected sum=63070	Resulted sum=63070	Expected cout=0	Resulted cout=0
Passed : a=63230 b=41570 cin=0	Expected sum=39264	Resulted sum=39264	Expected cout=1	Resulted cout=1
Passed : a=26608 b=46356 cin=0	Expected sum= 7428	Resulted sum= 7428	Expected cout=1	Resulted cout=1
Passed : a= 2550 b= 6566 cin=1	Expected sum= 9117	Resulted sum= 9117	Expected cout=0	Resulted cout=0
Passed : a=40473 b=62942 cin=1	Expected sum=37880	Resulted sum=37880	Expected cout=1	Resulted cout=1
Passed : a=22207 b=51851 cin=1	Expected sum= 8523	Resulted sum= 8523	Expected cout=1	Resulted cout=1
Passed : a=20532 b= 3901 cin=0	Expected sum=24433	Resulted sum=24433	Expected cout=0	Resulted cout=0
Passed : a=44421 b=40026 cin=0	Expected sum=18911	Resulted sum=18911	Expected cout=1	Resulted cout=1
Passed : a= 4538 b=40200 cin=1	Expected sum=44739	Resulted sum=44739	Expected cout=0	Resulted cout=0
Passed : a=36581 b=59827 cin=0	Expected sum=30872	Resulted sum=30872	Expected cout=1	Resulted cout=1
Passed : a=10184 b=41879 cin=0	Expected sum=52063	Resulted sum=52063	Expected cout=0	Resulted cout=0
Passed : a= 9900 b=39995 cin=1	Expected sum=49896	Resulted sum=49896	Expected cout=0	Resulted cout=0
Passed : a=16605 b=14773 cin=1	Expected sum=31379	Resulted sum=31379	Expected cout=0	Resulted cout=0
Passed : a=10010 b= 3486 cin=0	Expected sum=13496	Resulted sum=13496	Expected cout=0	Resulted cout=0
Passed : a=33126 b=35892 cin=1	Expected sum= 3483	Resulted sum= 3483	Expected cout=1	Resulted cout=1
Passed : a=34596 b= 8940 cin=0	Expected sum=43536	Resulted sum=43536	Expected cout=0	Resulted cout=0
Passed : a=43122 b=22569 cin=0	Expected sum= 155	Resulted sum= 155	Expected cout=1	Resulted cout=1
Passed : a=28635 b=13415 cin=0	Expected sum=42050	Resulted sum=42050	Expected cout=0	Resulted cout=0
Passed : a=54449 b=11863 cin=1	Expected sum= 777	Resulted sum= 777	Expected cout=1	Resulted cout=1
Passed : a= 8128 b=12287 cin=1	Expected sum=20416	Resulted sum=20416	Expected cout=0	Resulted cout=0
Passed : a=44328 b=47307 cin=0	Expected sum=26099	Resulted sum=26099	Expected cout=1	Resulted cout=1
Passed : a=16795 b=37384 cin=0	Expected sum=54179	Resulted sum=54179	Expected cout=0	Resulted cout=0
Passed : a=54866 b=49561 cin=1	Expected sum=38892	Resulted sum=38892	Expected cout=1	Resulted cout=1
Passed : a=62374 b=52415 cin=0	Expected sum=49253	Resulted sum=49253	Expected cout=1	Resulted cout=1
Passed : a= 2927 b=25097 cin=0	Expected sum=28024	Resulted sum=28024	Expected cout=0	Resulted cout=0
Passed : a=61930 b=30479 cin=0	Expected sum=26873	Resulted sum=26873	Expected cout=1	Resulted cout=1
Passed : a=38602 b=55767 cin=1	Expected sum=28834	Resulted sum=28834	Expected cout=1	Resulted cout=1
Passed : a=19349 b= 2427 cin=1	Expected sum=21777	Resulted sum=21777	Expected cout=0	Resulted cout=0
Passed : a=32554 b= 5497 cin=1	Expected sum=38052	Resulted sum=38052	Expected cout=0	Resulted cout=0
Passed : a=59048 b= 1054 cin=0	Expected sum=60102	Resulted sum=60102	Expected cout=0	Resulted cout=0
Passed : a=10376 b=47231 cin=1	Expected sum=57608	Resulted sum=57608	Expected cout=0	Resulted cout=0
Passed : a=25370 b=25425 cin=0	Expected sum=50795	Resulted sum=50795	Expected cout=0	Resulted cout=0
Passed : a= 8595 b=31130 cin=1	Expected sum=39726	Resulted sum=39726	Expected cout=0	Resulted cout=0
Passed : a=43675 b=48893 cin=1	Expected sum=27033	Resulted sum=27033	Expected cout=1	Resulted cout=1
Passed : a=59625 b=33668 cin=0	Expected sum=27757	Resulted sum=27757	Expected cout=1	Resulted cout=1
Passed : a= 3014 b= 5868 cin=0	Expected sum= 8882	Resulted sum= 8882	Expected cout=0	Resulted cout=0
Passed : a=44206 b= 5536 cin=0	Expected sum=49742	Resulted sum=49742	Expected cout=0	Resulted cout=0
Passed : a=33132 b=32155 cin=0	Expected sum=65287	Resulted sum=65287	Expected cout=0	Resulted cout=0
Passed : a=32863 b=31637 cin=1	Expected sum=64501	Resulted sum=64501	Expected cout=0	Resulted cout=0
Passed : a=15163 b= 3461 cin=0	Expected sum=18624	Resulted sum=18624	Expected cout=0	Resulted cout=0
Passed : a=51860 b= 6309 cin=1	Expected sum=58170	Resulted sum=58170	Expected cout=0	Resulted cout=0
Passed : a=42685 b=27565 cin=0	Expected sum= 4714	Resulted sum= 4714	Expected cout=1	Resulted cout=1
Passed : a=44336 b=11997 cin=0	Expected sum=56333	Resulted sum=56333	Expected cout=0	Resulted cout=0
Passed : a=23006 b=43606 cin=0	Expected sum= 1076	Resulted sum= 1076	Expected cout=1	Resulted cout=1

16-bit Carry Lookahead Adder with Generate Propagate Logic

```

Passed : a=36263 b=10770 cin=0 Expected sum=47033 Resulted sum=47033 Expected cout=0 Resulted cout=0
Passed : a= 7738 b=57586 cin=0 Expected sum=65324 Resulted sum=65324 Expected cout=0 Resulted cout=0
Passed : a=21413 b=20758 cin=0 Expected sum=42171 Resulted sum=42171 Expected cout=0 Resulted cout=0
Passed : a= 6224 b= 903 cin=1 Expected sum= 7128 Resulted sum= 7128 Expected cout=0 Resulted cout=0
Passed : a=13659 b=35858 cin=0 Expected sum=49517 Resulted sum=49517 Expected cout=0 Resulted cout=0
Passed : a=48189 b=48141 cin=0 Expected sum=30794 Resulted sum=30794 Expected cout=1 Resulted cout=1
Passed : a= 336 b=36506 cin=0 Expected sum=36842 Resulted sum=36842 Expected cout=0 Resulted cout=0
Passed : a=13382 b=32483 cin=1 Expected sum=45866 Resulted sum=45866 Expected cout=0 Resulted cout=0
Passed : a= 7232 b=41697 cin=0 Expected sum=48929 Resulted sum=48929 Expected cout=0 Resulted cout=0
Passed : a=64263 b=18324 cin=1 Expected sum=17052 Resulted sum=17052 Expected cout=1 Resulted cout=1
Passed : a=54537 b=32311 cin=1 Expected sum=21313 Resulted sum=21313 Expected cout=1 Resulted cout=1
Passed : a=24703 b=55519 cin=0 Expected sum=14686 Resulted sum=14686 Expected cout=1 Resulted cout=1
Passed : a=48032 b=55090 cin=0 Expected sum=37586 Resulted sum=37586 Expected cout=1 Resulted cout=1
Passed : a=14669 b=31043 cin=0 Expected sum=45712 Resulted sum=45712 Expected cout=0 Resulted cout=0
Passed : a=35023 b=16696 cin=1 Expected sum=51720 Resulted sum=51720 Expected cout=0 Resulted cout=0
Passed : a=56312 b=41318 cin=0 Expected sum=32094 Resulted sum=32094 Expected cout=1 Resulted cout=1
Passed : a=55512 b=59165 cin=1 Expected sum=49142 Resulted sum=49142 Expected cout=1 Resulted cout=1
Passed : a= 5220 b=43474 cin=1 Expected sum=48695 Resulted sum=48695 Expected cout=0 Resulted cout=0
Passed : a= 686 b= 175 cin=1 Expected sum= 862 Resulted sum= 862 Expected cout=0 Resulted cout=0
Passed : a=22023 b= 7522 cin=1 Expected sum=29546 Resulted sum=29546 Expected cout=0 Resulted cout=0
Passed : a=20943 b=29783 cin=0 Expected sum=50726 Resulted sum=50726 Expected cout=0 Resulted cout=0
Passed : a=13965 b=26633 cin=1 Expected sum=40599 Resulted sum=40599 Expected cout=0 Resulted cout=0
Passed : a=37434 b=64092 cin=0 Expected sum=35990 Resulted sum=35990 Expected cout=1 Resulted cout=1
Passed : a= 1386 b=24640 cin=1 Expected sum=26027 Resulted sum=26027 Expected cout=0 Resulted cout=0
Passed : a=21142 b=46591 cin=0 Expected sum= 2197 Resulted sum= 2197 Expected cout=1 Resulted cout=1
Passed : a=22997 b=61082 cin=1 Expected sum=18544 Resulted sum=18544 Expected cout=1 Resulted cout=1
Passed : a=18644 b=10193 cin=1 Expected sum=28838 Resulted sum=28838 Expected cout=0 Resulted cout=0
Passed : a=43483 b=17386 cin=0 Expected sum=60869 Resulted sum=60869 Expected cout=0 Resulted cout=0
Passed : a=38097 b=33929 cin=1 Expected sum= 6491 Resulted sum= 6491 Expected cout=1 Resulted cout=1
Passed : a=61030 b=31104 cin=1 Expected sum=26599 Resulted sum=26599 Expected cout=1 Resulted cout=1

```

```

-----Coverage Results-----

# of Case Tested for Type 1: (CV)='00'=261 cases with percentage=52.200000, Pass rate=100.000000, Fail rate=0.000000
# of Case Tested for Type 2: (CV)='01'=0 cases with percentage=0.000000, Pass rate=-nan, Fail rate=-nan
# of Case Tested for Type 3: (CV)='10'=0 cases with percentage=0.000000, Pass rate=-nan, Fail rate=-nan
# of Case Tested for Type 4: (CV)='11'=239 cases with percentage=47.800000, Pass rate=100.000000, Fail rate=0.000000
Total Coverage pass rate = 100.00 %

-----Coverage Results End-----

Simulation complete via $finish(1) at time 5015 NS + 1
../testbench/environment.sv:35      $finish;
ncsim> exit

```

The Report explicitly shows that a coverage of 100% is achieved.

7. Step-4 (Synthesis with Optimized Power, Performance & Area)

.tcl code for varying input delay

```

# Run Genus in Legacy UI if Genus is invoked with Common UI

::legacy::set_attribute common_ui false /

```



```

# CPU Info check (optional)
if {[file exists /proc/cpuinfo]} {
    sh grep "model name" /proc/cpuinfo
    sh grep "cpu MHz" /proc/cpuinfo
}

# Print hostname (optional)
puts "Hostname : [info hostname]"

#####

### Preset global variables and attributes
#####

# Set input_delay times to iterate over
set input_delays {0.2 0.3 0.4 0.5 0.6}

set DESIGN cla16
set SYN_EFF low
set MAP_EFF low
set OPT_EFF low

# Directory of PDK
set pdk_dir /home/cad/VLSI2Lab/Digital/library/
set_attribute init_lib_search_path $pdk_dir

# Set synthesizing effort for each synthesis stage
set_attribute syn_generic_effort $SYN_EFF
set_attribute syn_map_effort $MAP_EFF
set_attribute syn_opt_effort $OPT_EFF
set_attribute library "slow_vdd1v0_basicCells.lib"

```

```

# Avoid using specific library cells
set_dont_use [get_lib_cells CLK*]
set_dont_use [get_lib_cells SDFF*]
set_dont_use [get_lib_cells DLY*]
set_dont_use [get_lib_cells HOLD*]

# Load Design
read_hdl "${DESIGN}.v"
elaborate $DESIGN
check_design -unresolved

# Iterate over each input delay
foreach input_delay $input_delays {
    # Create a new SDC file for each input_delay time
    set sdc_file "${DESIGN}_input_delay_${input_delay}_low.sdc"

    # Open the SDC file for writing
    set output [open $sdc_file "w"]
    puts $output "set setup_time 0.3"
    puts $output "create_clock -period 10 -waveform {0 6} -name func_clk [get_ports clk]"

    # Writing SDC constraints to the file
    #puts $output "set input_delay ${input_delay}"
    puts $output "set_input_delay ${input_delay} -clock [get_clocks func_clk] {A B Cin}"
    puts $output "set_output_delay 0.6 -clock [get_clocks func_clk] {Cout Sum}"

    puts $output "set_hold_time 0.2 -clock [get_clocks func_clk] {A B Cin}"

    # Closing the SDC file after writing
    close $output
}

```

```

# Read the newly created SDC file
read_sdc $sdc_file

# Run synthesis with the newly set constraints
syn_generic

puts "Runtime & Memory after 'syn_generic' for input delay time ${input_delay} ns"
time_info GENERIC

# Generate report after synthesis
report_power -verbose -detail >> reports/power_report_input_delay_${input_delay}_low.txt
report_area >> reports/area_report_input_delay_${input_delay}_low.txt

# Synthesize to mapped design
synthesize -to_mapped

write -mapped > ${DESIGN}_synth_input_delay_${input_delay}_low.v
}

# Final script for execution
write_script > script

```

Data for Low Effort

Setup Time(.3)

Value	Area	Leakage Power	Internal Power	Net Power	Dynamic Power	Total Power
.1	612	5.625	5046.076	4345.144	9391.22	9396.845
.2	478	4.899	4832.767	3737.644	8570.411	8575.309
.3	487	5.072	5099.365	3714.862	8814.228	8819.30
.4	288	4.245	5849.826	2572.003	8421.829	8426.073
.5	275	4.201	5945.181	2466.956	8412.137	8416.339

Hold Time(ns)

Value	Area	Leakage Power	Internal Power	Net Power	Dynamic Power	Total Power
.1	612	5.625	5046.076	4345.144	9391.22	9396.845
.2	478	4.899	4832.767	3737.644	8570.411	8575.309
.3	487	5.072	5099.365	3714.862	8814.228	8819.30
.4	288	4.245	5849.826	2572.003	8421.829	8426.073
.5	275	4.201	5945.181	2466.956	8412.137	8416.339

Clock Period(ns)

Value	Area	Leakage Power	Internal Power	Net Power	Dynamic Power	Total Power
5	612	5.625	5046.076	4345.144	9391.22	9396.845
10	478	4.899	4832.767	3737.644	8570.411	8575.309
15	487	5.072	5099.365	3714.862	8814.228	8819.30
20	288	4.245	5849.826	2572.003	8421.829	8426.073
25	275	4.201	5945.181	2466.956	8412.137	8416.339

Input Delay(ns)

Value	Area	Leakage	Internal	Net	Dynamic	Total Power
.3	612	5.625	5046.076	4345.144	9391.22	9396.845
.4	478	4.899	7142.693	5636.081	12778.774	12783.673
.5	487	5.072	7583.01	5613.933	13196.943	13202.015
.6	288	4.245	8615.366	3602.222	12217.587	12221.832
.7	275	4.201	8742.557	3471.23	12213.787	12217.988

Output Delay(ns)

Value	Area	Leakage Power	Internal Power	Net Power	Dynamic Power	Total Power
.5	612	5.625	5046.076	4345.144	9391.22	9396.845
.6	478	4.899	4832.767	3737.644	8570.411	8575.309
.7	487	5.072	5099.365	3714.862	8814.228	8819.30
.8	288	4.245	5849.826	2572.003	8421.829	8426.073
.9	275	4.201	5945.181	2466.956	8412.137	8416.339


*All Power components are in nW unit

Data for High & Medium Effort


We have achieved the same sort of data for low, Medium and high effort.

Plots


Area vs. Time:

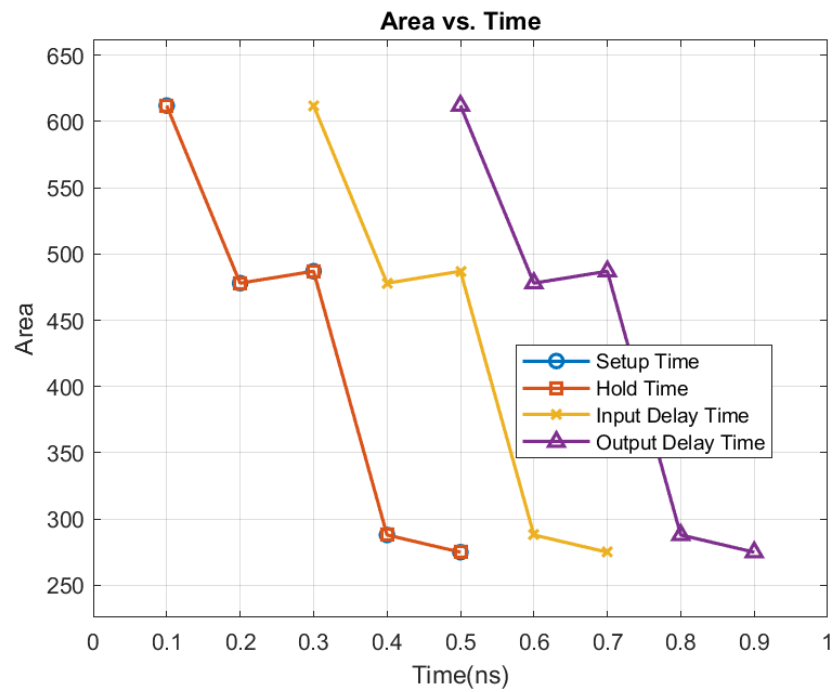


Leakage Power vs. Time:

 


Internal Power vs. Time

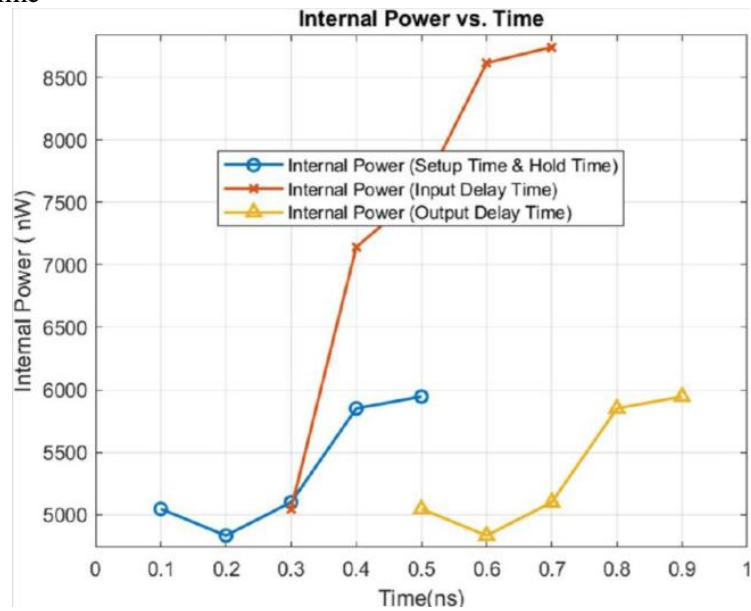

Net Power vs. Time

 


Total Power vs. Time:

 

Analyzing these data, we have selected the following parameters for better PPA optimization:
Hold time = 0.2ns, Setup time = 0.3ns, Clock Frequency = 100MHz, Input delay = 0.4ns, Output delay = 0.6ns.

Synthesized Design

 


8. Step-5 (Optimized Physical Design with respect to Die Size, Pin Planning, and Power Rails)

Final design


Layout (After Adding Pins)




Layout (After Adding Power Strips)

 


Layout (Adding Rails)

 


Layout (Cell Placement)

 

Layout (After Nano Routing)

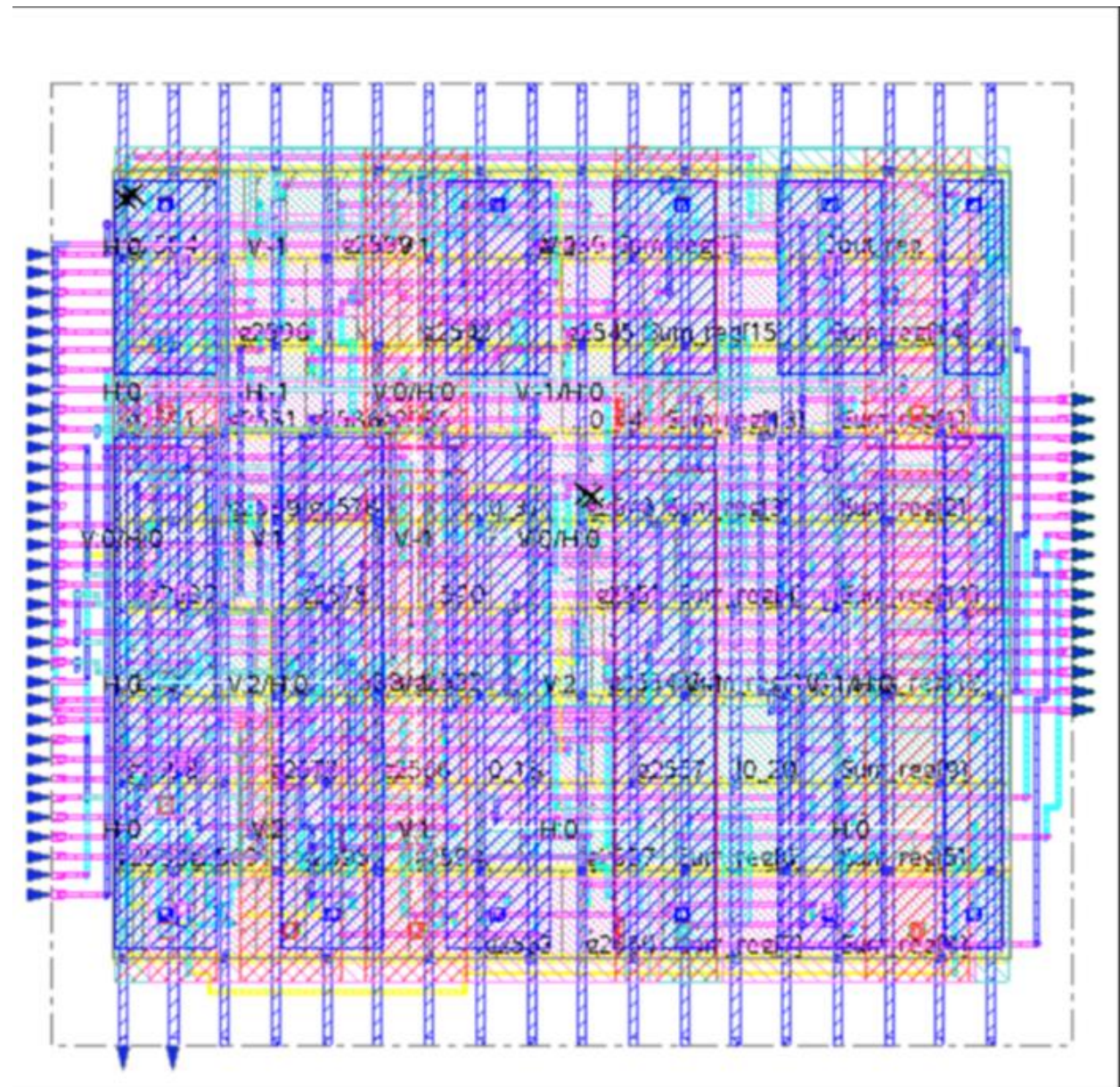

Layout (Final)

 

Summary Reports

----- optDesign Final SI Timing Summary -----				
Setup views included: func@BC_rcbest0.hold				
Hold views included: func@BC_rcbest0.hold				
Setup mode	all	reg2reg	default	
WNS (ns):	9.022	N/A	9.022	
TNS (ns):	0.000	N/A	0.000	
Violating Paths:	0	N/A	0	
All Paths:	18	N/A	18	
Hold mode	all	reg2reg	default	
WNS (ns):	0.035	N/A	0.035	
TNS (ns):	0.000	N/A	0.000	
Violating Paths:	0	N/A	0	
All Paths:	18	N/A	18	
DRVs	Real		Total	
	Nr nets(terms)	Worst Vio	Nr nets(terms)	
max_cap	0 (0)	0.000	0 (0)	
max_tran	0 (0)	0.000	0 (0)	
max_fanout	0 (0)	0	0 (0)	
max_length	0 (0)	0	0 (0)	
Density: 79.798%				
Total number of glitch violations: 0				

This report shows that –

- Setup and hold time constraints are met (as there is no negative slack time).
- There are no DRV (Design Rule Violations).
- The density of **79.798%** indicates a moderately high utilization of the available chip area. While further optimization could potentially increase density, keeping it below **80%** ensures practical design feasibility.
- No glitch violations detected, meaning stable and glitch-free logic transitions.

Timing Report

```
innovus 17> report_timing
#####
# Generated by: Cadence Innovus 16.10-p004_1
# OS: Linux x86_64(Host ID CadenceServer3.localdomain)
# Generated on: Mon Dec 16 13:40:04 2024
# Design: clal6
# Command: report_timing
#####
Path 1: MET Setup Check with Pin Cout_reg/CK
Endpoint: Cout_reg/D (^) checked with leading edge of 'func_clk'
Beginpoint: Cin (^) triggered by leading edge of 'func_clk'
Path Groups: {func_clk}
Analysis View: func@BC_rcbest0.hold
Other End Arrival Time -0.000
- Setup 0.025
+ Phase Shift 10.000
= Required Time 9.975
- Arrival Time 0.966
= Slack Time 9.009

Clock Rise Edge 0.000
+ Input Delay 0.400
= Beginpoint Arrival Time 0.400
+-----+
| Instance | Arc | Cell | Delay | Arrival | Required |
|-----|-----|-----|-----|-----|-----|
| | Cin ^ | | | 0.400 | 9.409 |
| g2583 | A1 ^ -> Y v | AOI22X1 | 0.030 | 0.430 | 9.439 |
| g2580 | A1 v -> Y ^ | OAI21X1 | 0.035 | 0.465 | 9.474 |
| g2577 | A1 ^ -> Y v | AOI22X1 | 0.037 | 0.502 | 9.512 |
| g2574 | A1 v -> Y ^ | OAI21X1 | 0.035 | 0.537 | 9.546 |
| g2571 | A1 ^ -> Y v | AOI22X1 | 0.036 | 0.573 | 9.582 |
| g2568 | A1 v -> Y ^ | OAI21X1 | 0.035 | 0.608 | 9.618 |
| g2565 | A1 ^ -> Y v | AOI22X1 | 0.038 | 0.646 | 9.655 |
| g2562 | A1 v -> Y ^ | OAI21X1 | 0.035 | 0.681 | 9.690 |
| g2559 | A1 ^ -> Y v | AOI22X1 | 0.037 | 0.718 | 9.728 |
| g2556 | A1 v -> Y ^ | OAI21X1 | 0.035 | 0.753 | 9.762 |
| g2553 | A1 ^ -> Y v | AOI22X1 | 0.037 | 0.790 | 9.799 |
| g2550 | A1 v -> Y ^ | OAI21X1 | 0.035 | 0.825 | 9.834 |
| g2547 | A1 ^ -> Y v | AOI22X1 | 0.037 | 0.862 | 9.872 |
| g2544 | A1 v -> Y ^ | OAI21X1 | 0.035 | 0.897 | 9.907 |
| g2541 | A1 ^ -> Y v | AOI22X1 | 0.037 | 0.934 | 9.944 |
| g2538 | A1 v -> Y ^ | OAI21X1 | 0.032 | 0.966 | 9.975 |
| Cout_reg | D ^ | DFFHQX1 | 0.000 | 0.966 | 9.975 |
+-----+
```

This report shows that –

- Clock propagation is detected successfully.
- Setup timing is matches as WNS (Worst Negative Slack) is positive.

DRC result

```
Total CPU Time : 1 (s)
Total Real Time : 1 (s)
Peak Memory Used : 20 (M)
Total Original Geometry : 1479 (9906)
Total DRC RuleChecks : 562
Total DRC Results : 0 (0)
Summary can be found in file clal6.sum
ASCII report database is /home/vlsil2/eee468_G1_G12/synthesis/clal6.drc_errors.ascii
Checking in all softshare licenses.
```

This result indicates –

- A clean layout as no DRC violations were found.
- The design is efficient in computation and moderate in complexity.

9. Conclusion

In conclusion, the 16-bit Carry Lookahead Adder with Generate-Propagate Logic was successfully designed and implemented to reduce the delay caused by carry propagation, making it faster than traditional adders. The design was optimized for delay, power use, and area, making it suitable for high-performance digital systems. Simulations and tests confirmed that the adder works correctly and efficiently, showing its potential for use in larger circuits like multipliers and ALUs. This project demonstrates how advanced design methods can improve the performance of modern VLSI systems.

10. Links of Codes and Files

- Layered Testbench: <https://edaplayground.com/x/s4Q>
- Directed Testbench: <https://edaplayground.com/x/HAfM>
- Theory: *Hierarchical carry lookahead adder*.
https://www2.cs.sfu.ca/CourseCentral/150/eyal/lectures/CLA.pdf?fbclid=IwY2xjawHPRzxleHRuA2FlbQlXMAABHevx9r-I4Z8FY82nj37Ccxvs5QwHa25t1dropoFzzizV3uBok5qZ9WZESA_aem_5uCWPh-03y4GOrDOEDN2-A